

Section 1: Signed Numbers and Patterns - /30 Points

1. What is the maximum number of patterns able to be stored in a 5-bit number? How many of those patterns represent negative numbers in 2's Complement?
2. Convert the following to **4-bit Signed Magnitude**:
 - a) -5
 - b) -7
 - c) +6
3. Convert the following to **4-bit 1's Complement**:
 - a) -3
 - b) -9
 - c) -1
4. Convert the following to **4-bit 2's Complement**:
 - a) -4
 - b) -7
 - c) -1
5. Convert the following 4-bit 2's Complement numbers back to base-10:
 - a) 1101
 - b) 1000
 - c) 1011
6. Perform **4-bit 2's Complement addition** on the following. Identify whether overflow occurs:
 - a) $-3 + 5$
 - b) $-6 + -4$
 - c) $7 + 2$
7. Perform **4-bit 2's Complement subtraction** on the following. Remember: $a - b = a + -(b)$
 - a) $5 - 3$
 - b) $2 - 6$
 - c) $-4 - 3$
8. You are given an encoding scheme that maps 3-bit patterns to the following values:

Binary	Encoded Value
000	A
001	B
010	C
011	D
100	E
101	F
110	G
111	H

- a) How many patterns are available?
- b) If you increment the binary 111 by 1, what happens? What is this called? If we read 111 as the encoding and then added 1, what transition of the symbols would occur?
- c) If you needed to encode 10 distinct values, what is the minimum number of bits required?

Section 2: Boolean Logic and Gates - /20 points

1. Write the boolean expression for each of the following gate combinations (simplify if you can):
 - a) NOT(A AND B)
 - b) (A OR B) AND (NOT A)
 - c) NOT(NOT A AND NOT B)
2. Convert the following boolean expressions to circuit diagrams (draw the gates and label all wires):
 - a) $Out = (A \text{ AND } B) \text{ OR } (\text{NOT } A \text{ AND } C)$
 - b) $Out = \text{NOT}(A \text{ OR } B) \text{ AND } C$

- c) $\text{Out} = A \text{ XOR } (B \text{ AND } C)$

3. Explain in 1-2 sentences what **functional completeness** means, and give an example of a functionally complete set of gates.
4. Show how to build an **AND gate** using only NAND gates. Provide the circuit diagram and verify with a truth table.
5. Show how to build an **OR gate** using only NAND gates.

Section 3: Truth Tables to Circuits - /20 points

1. Implement the following truth table into a circuit. Derive the boolean expression first, then draw the circuit:

A	B	C	Out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

1. Implement the following two-output truth table into a circuit. Derive boolean expressions for **each output separately**:

A	B	C	Out1	Out2
0	0	0	1	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	0	1

- Hint: Look at what patterns each output follows relative to the inputs. Do any familiar operations come to mind?

Section 4: Basic Circuits - /20 points

1. Draw the truth table for a **Half Adder**. Label the outputs **Sum** and **Carry**. What basic gates make up a half adder?
2. Explain in your own words why a **Full Adder** is needed over a Half Adder. What extra input does it have and what is it used for?
3. Given a **Ripple Carry Adder** built from full adders:
 - a) How many full adders would you need to add two 8-bit numbers?
 - b) Why is it called a "ripple carry" adder?
 - c) What happens if the final carry-out is 1 when working in 2's Complement?
 - Fill in the output column of the following **MUX truth table** (2-to-1 MUX with select line S, inputs A and B):

S	A	B	Out
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Write the boolean expression for a 2-to-1 MUX.

1. A **2-to-4 Decoder** takes a 2-bit input and activates exactly one of 4 output lines. Fill in its truth table and write the boolean expression for each output line:

A	B	Out0	Out1	Out2	Out3
0	0				
0	1				
1	0				
1	1				

Section 5: Design Problems - /25 points

1. Design a **2-bit ALU** with 3 operations controlled by a 2-bit Op signal. Inputs are 2-bit numbers A and B:

- Op = 00 : Output A AND B (bitwise)
- Op = 01 : Output A OR B (bitwise)
- Op = 10 : Output A + B (addition, ignore carry-out)

You may use circuit symbols for Half/Full Adders and MUXes. Label all input/output lines and control signals.

2. Design a circuit that takes a 2-bit binary number as input and outputs its **2's Complement negation** as a 2-bit number (ignore overflow). Show your work:

- a) Write out the truth table for all input combinations
- b) Derive the boolean expression for each output bit
- c) Draw the circuit
- A **4-bit Ripple Carry Adder** is used to add two 4-bit 2's Complement numbers.
- a) What is the range of numbers each input can represent?
- b) Add 0111 + 0001 . Does overflow occur? How can you detect overflow in a 2's Complement adder?
- c) Add 1010 + 1101 . What is the result in base-10?

Point Summary

Section	Points
Section 1: Signed Numbers and Patterns	/30
Section 2: Boolean Logic and Gates	/20
Section 3: Truth Tables to Circuits	/20
Section 4: Basic Circuits	/20
Section 5: Design Problems	/25
Total	/115